

Lab 2 – Liquid Crystal Display (LCD)

Graduate Teaching Assistant:

Francisco E. Fernandes Jr.

feferna@okstate.edu

**School of Electrical and Computer Engineering
Oklahoma State University**

Fall 2018








Grading Rubrics and Schedule



- **Pre-lab assignment:**
 - Due on September 24, 2018: 10 points.
- **In-lab assignment (total of 70 points):**
 - **September 24, 2018:**
 - Write code for `LCD_PIN_Init()` – 10 points
 - **October 01, 2018:**
 - Write code for `LCD_Configuration()` – 30 points
 - **October 08, 2018:**
 - Write code for `LCD_Display_Name()` – 20 points
 - Answer lab demonstration question – 10 points
- **Post-lab assignment (total of 20 points):**
 - Due on October 15 on Dropbox:
 - Your Keil uVision Project: 10 points
 - Answers for Post-lab questions: 10 points

You will be
graded EVERY
CLASS!

Types of LCD

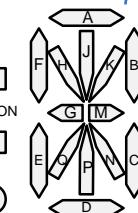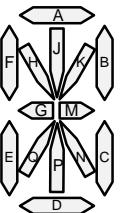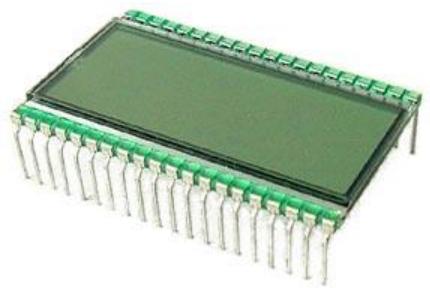

Segment LCD

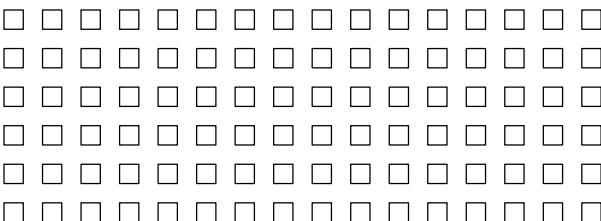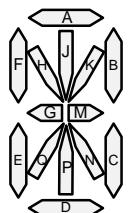


Dot Matrix LCD




Multiplexed LCD drive

Duty Ratio

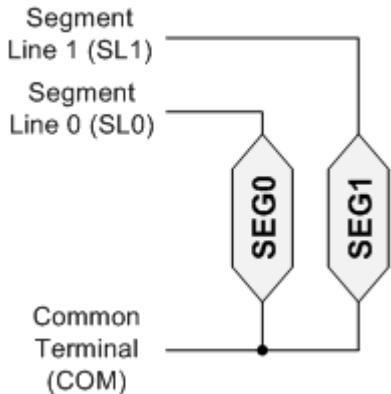
- how long each segment is activated during each frame



Duty = 1

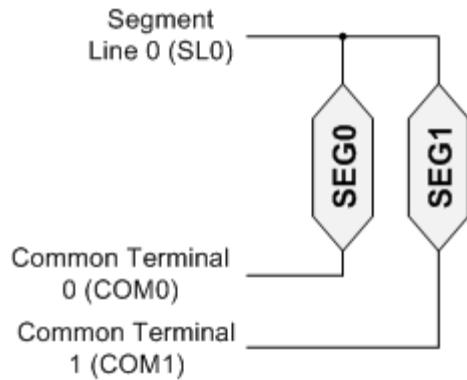

Duty = 1/2

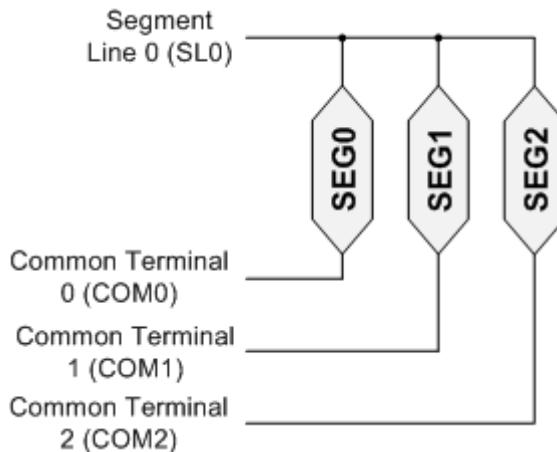

Duty = 1/3

$$\text{Duty Ratio} = \frac{1}{\text{Number of Common Terminals}}$$


Drive Bias

- the number of voltage levels used


$$\text{Bias} = \frac{1}{\text{Number of Voltage Levels} - 1}$$

Multiplexed LCD drive

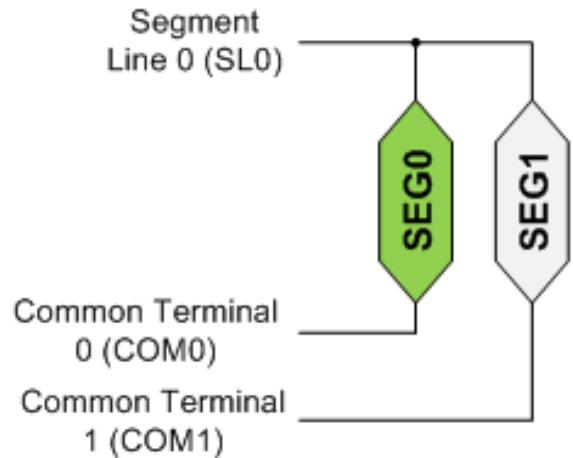Duty Ratio = $\frac{1}{2}$, SEG0 ON, SEG1 OFF




SEG0 is switched on and off quickly.

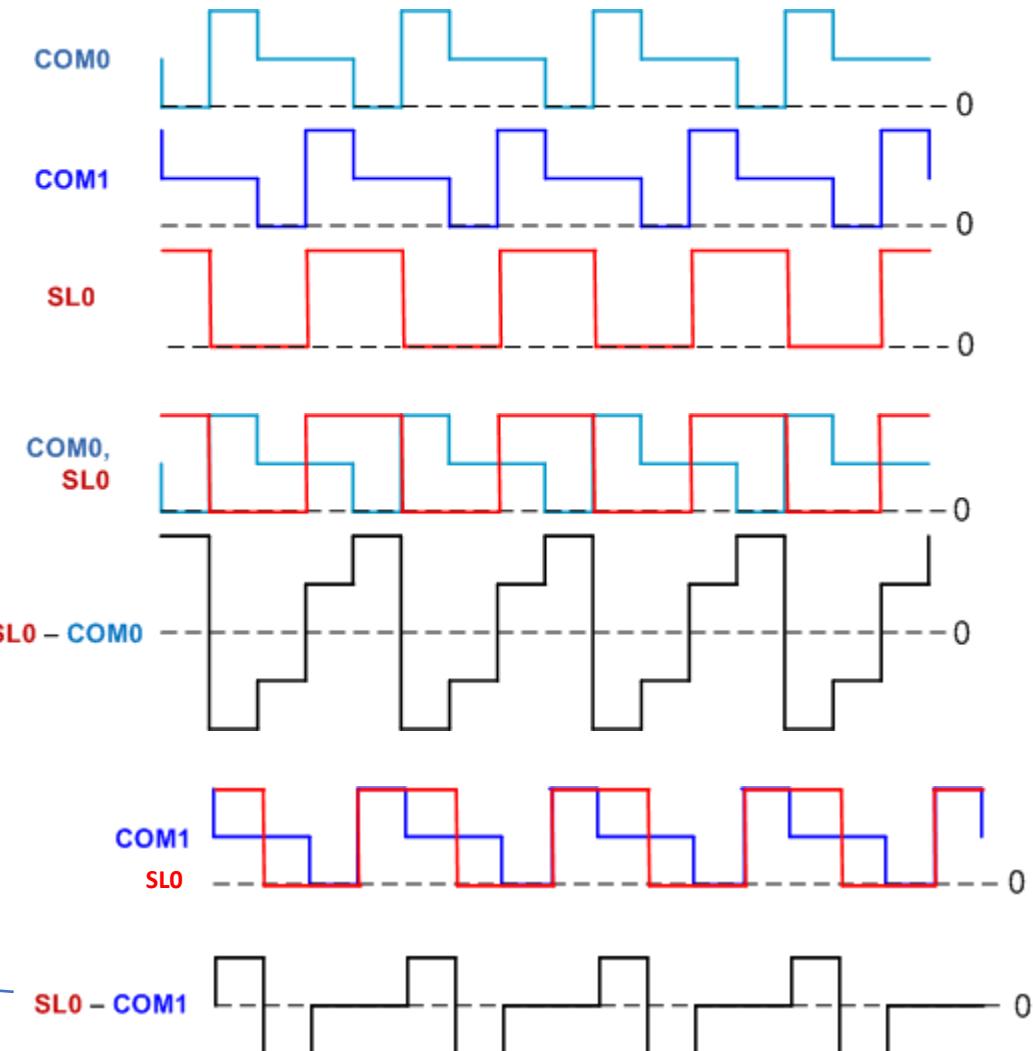

SEG1 will never turn on.


Multiplexed LCD drive

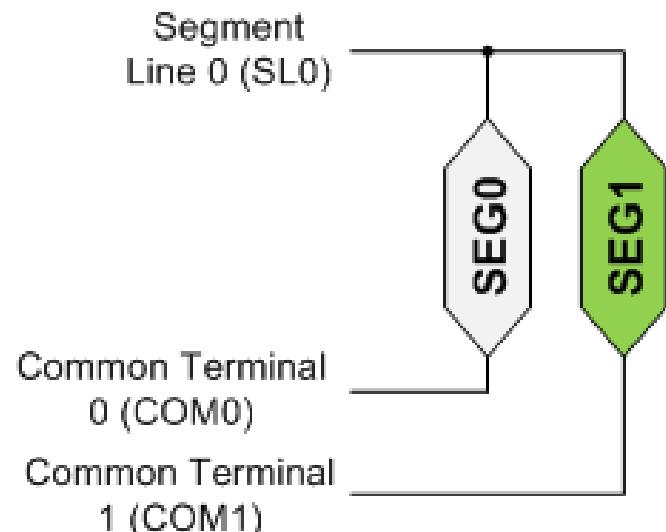Duty Ratio = $\frac{1}{2}$, SEG0 OFF, SEG1 ON



SEG0 will never turn on!

SEG1 is switched on
and off quickly.

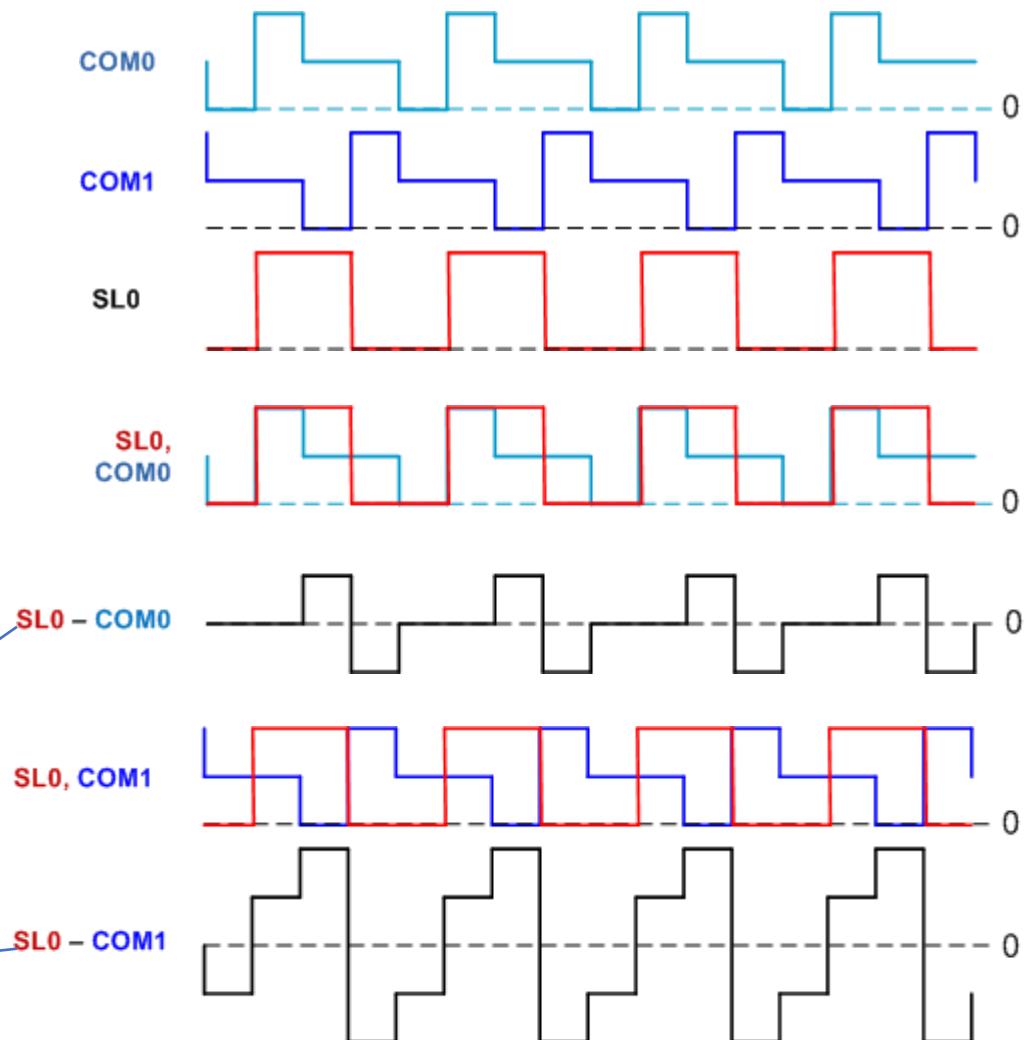

LCD on the ST32L4 Discovery Kit




Duty Ratio = $\frac{1}{4}$

24 segment lines
(SEG0-SEG23)

4 common terminals
(COM0-COM3)

6 digits and **4** bars

96 pixel segments

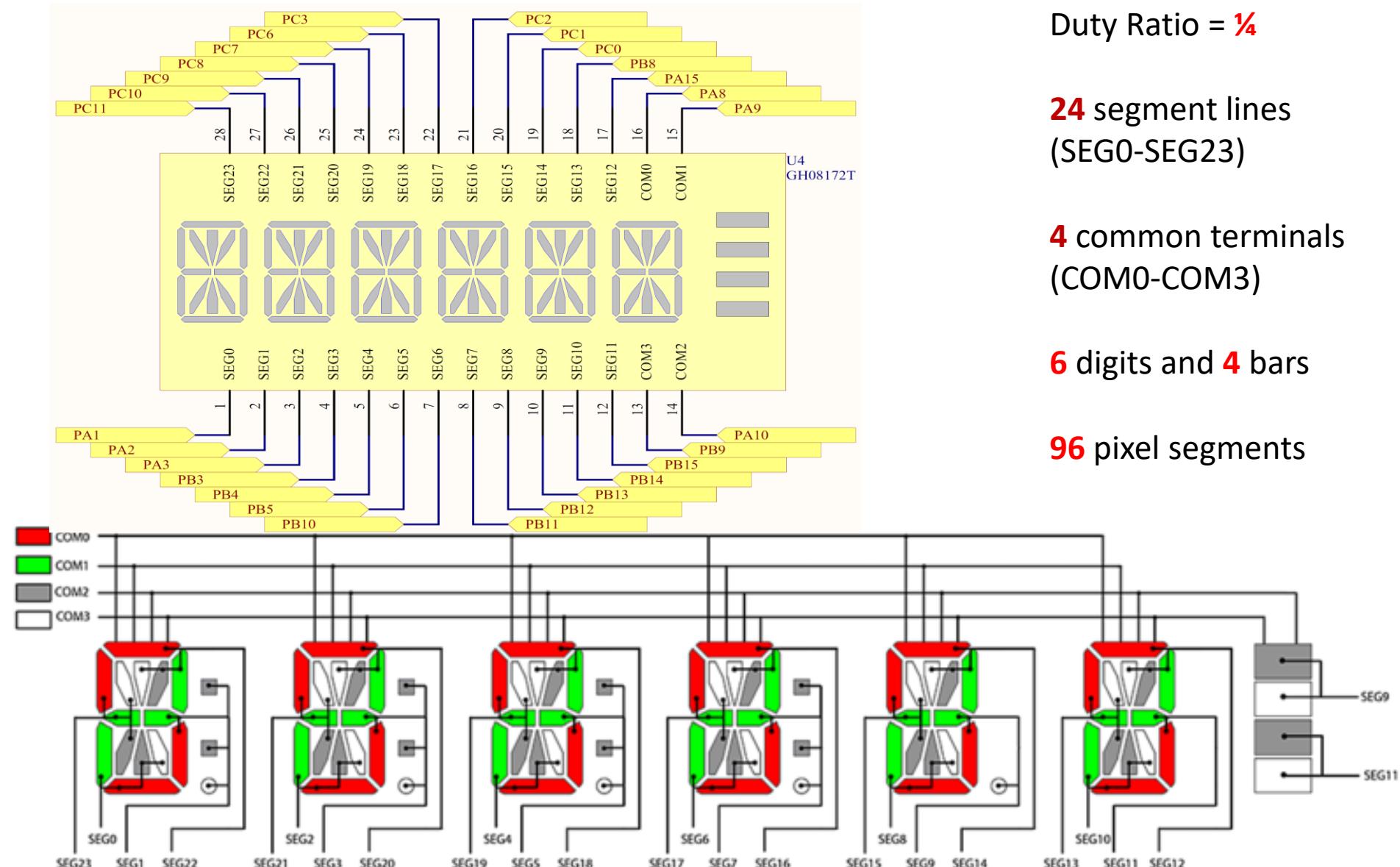




Lab Assignment

- The basic requirement of this lab is to display your last name on the LCD.
- You are provided with a startup Keil uVision Project containing **main.c**, **LCD.c**, and **LCD.h** files.
- You are only required to write code in the **LCD.c** file. You must implement three functions inside **LCD.c**:
 - **10 points:** *LCD_PIN_Init()* – Due on **Sept. 24**.
 - **30 points:** *LCD_Configure()* – Due on **Oct. 01**.
 - **20 points:** *LCD_Display_Name()* – Due on **Oct. 08**.
 - **10 points:** **Lab demo questions** – Due on **Oct. 08**.

Lab flowchart

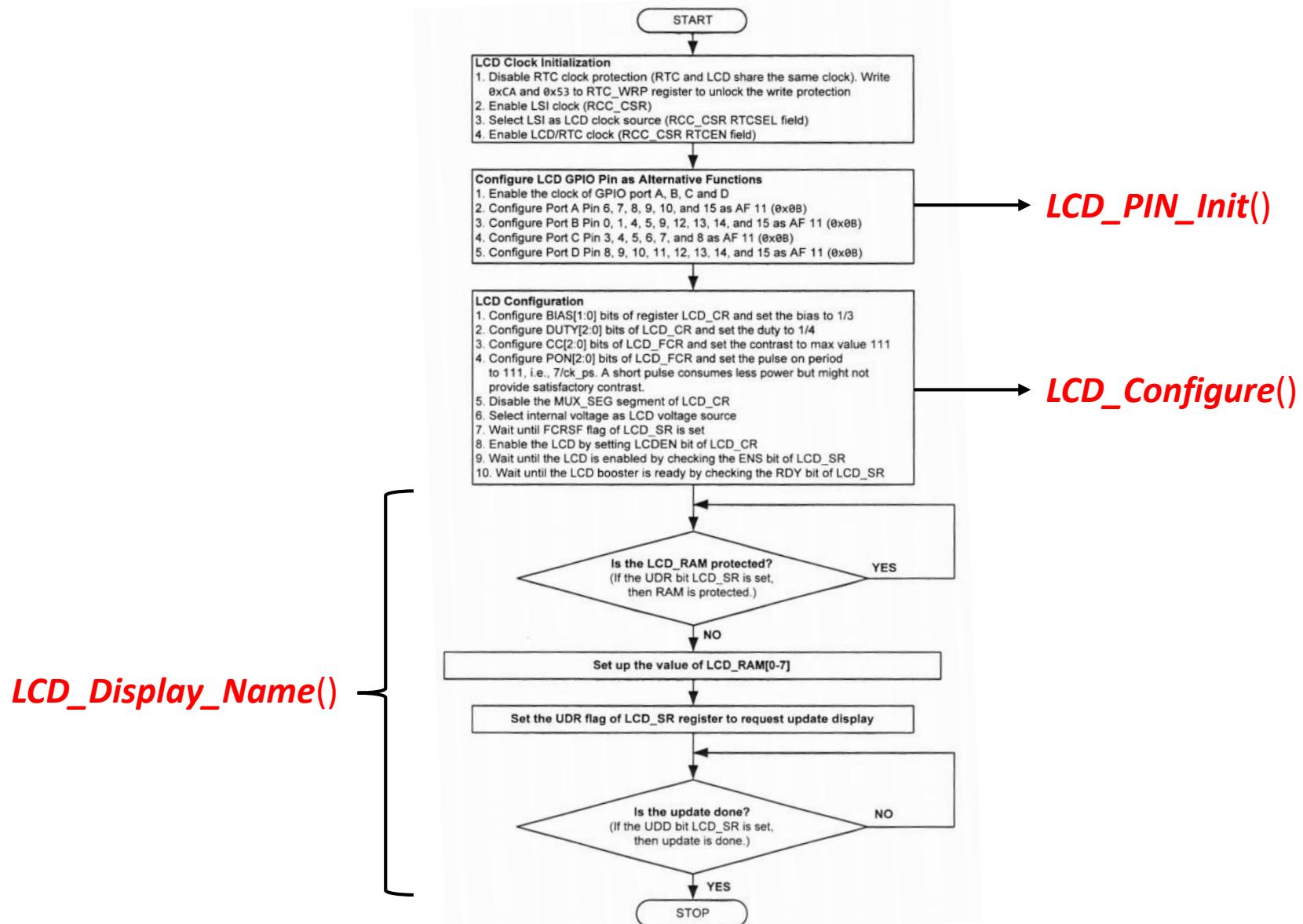

LCD_PIN_Init()



1. Enable the clock of GPIO port A, B, C and D.
2. Configure PA 6, 7, 8, 9, 10, 15 as Alternative Function 11 (0x0B).
3. Configure PB 0, 1, 4, 5, 9, 12, 13, 14, 15 as Alternative Function 11 (0x0B).
4. Configure PC 3, 4, 5, 6, 7, 8 as Alternative Function 11 (0x0B).
5. Configure PD 8, 9, 10, 11, 12, 13, 14, 15 as Alternative Function 11 (0x0B).

```
GPIOx->MODER &= ~MASK;  
GPIOx->MODER |= MASK;
```

```
GPIOx->AFR[0] &= ~MASK;  
GPIOx->AFR[0] |= MASK;
```

```
GPIOx->AFR[1] &= ~MASK;  
GPIOx->AFR[1] |= MASK;
```

```
GPIOx->OSPEEDR &= ~(MASK);
```

```
// GPIOx Push-Pull: No pull-up, pull-down (00)  
GPIOx->PUPDR &= ~MASK;
```



LCD_Configure()

```
// 1. Configure BIAS[1:0] bits of register LCD_SR and set the bias to 1/3
LCD->CR ; //BIAS[1:0]: 00=1/4; 01=1/2; 10=1/3

// 2. Configure DUTY[2:0] bits of LCD_CR and set the duty to 1/4
LCD->CR ; //DUTY[2:0]: 000=Static; 001=1/2; 010=1/3; 011=1/4; 100=1/8

// 3. Configure CC[2:0] bits of LCD_FCR and set the contrast to max value 111
LCD->FCR ;

// 4. Configure PON[2:0] bits of LCD_FCR and set the pulse on period to 111.
LCD->FCR ; // PON[2:0] = 0x111

// 5. Diable the MUX_SEG segment of LCD_CR
LCD->CR ;

// 6. Select internal voltage as LCD voltage source
LCD->CR ; // 0 = internal source, 1 = external source (VLCD pin)

// 7. Wait until FCRSF flag of LCD_SR is set
while ((LCD->SR & MASK) == 0); // Wait until FCRSF flag is set

// 8. Enable the LCD by setting LCDEN bit of LCD_CR
LCD->CR ;

// 9. Wait until the LCD is enabled by checking the ENS bit of LCD_SR
while ((LCD->SR & MASK) == 0); // ENS is set by hardware automatically

// 10. Wait until the LCD booster is ready by checking the RDY bit of LCD_SR
while ((LCD->SR & MASK) == 0); // Loop until step-up converter is ready to provide the correct voltage.
```



LCD_Configure()

Use the LCD
Register Map in
order to find the
correct bit
positions!

Offset	Register	31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
0x00	LCD_CR	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.		
		Reset value																															
0x04	LCD_FCR	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.			
		Reset value																															
0x08	LCD_SR	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.			
		Reset value																															
0x0C	LCD_CLR	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.	Res.			
		Reset value																															




LCD_Display_Name()

```
// Is the LCD_RAM protected?  
// If the UDR bit in LCD_SR is set, then RAM is protected  
while ((LCD->SR & MASK) != 0); // Wait for Update Display Request Bit  
  
// Set up the value of LCD_RAM[0-7] with your last name  
LCD->RAM[0] ;  
LCD->RAM[1] ;  
LCD->RAM[2] ;  
LCD->RAM[3] ;  
LCD->RAM[4] ;  
LCD->RAM[5] ;  
LCD->RAM[6] ;  
LCD->RAM[7] ;  
  
// Set the UDR flag of LCD_SR register to request update display  
LCD->SR |= MASK;  
  
// Is the update done?  
// If the UDD bit in LCD_SR is set, then update is done.  
while ((LCD->SR & MASK) == 0); // Wait for update display done
```



LCD_Display_Name()

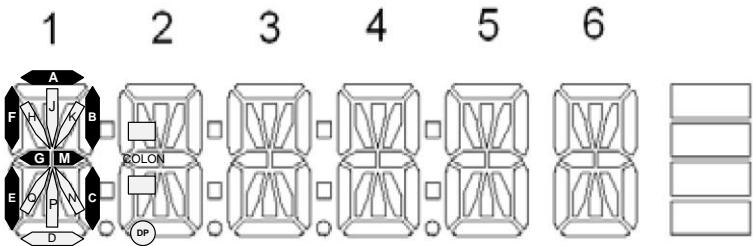

// Set up the value of LCD_RAM[0-7] with your last name

LCD->RAM[0] |= 0x00C00018;

LCD->RAM[2] |= 0x00C00008;

	31	30	29	28	27	26	25	24	23	22	21	20	19	18	17	16	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
LCD_RAM[0]	4E	4G	3M	3B		6G	5M	5B	1M	1B					6E		3E	3G	2M	2B			6B	6M		2E	2G	1E	1G			
LCD_RAM[1]																												5E	5G	4M	4B	
LCD_RAM[2]	4D	4F	3C	3A		6F	5C	5A	1C	1A					6D		3D	3F	2C	2A			6A	6C		2D	2F	1D	1F			
LCD_RAM[3]																												5D	5F	4C	4A	
LCD_RAM[4]	4P	4Q	3 Col	3K		6Q	3 Bar	5K	1 Col	1K					6P		3P	3Q	2 Col	2K			6K	1 Bar		2P	2Q	1P	1Q			
LCD_RAM[5]																												5P	5Q	4 Col	4K	
LCD_RAM[6]	4N	4H	3 DP	3J		6H	2 Bar	5J	1 DP	1J					6N		3N	3H	2 DP	2J			6J	0 Bar		2N	2H	1N	1H			
LCD_RAM[7]																												5N	5H	4 DP	4J	